


## MY00 STI central locking...

The central locking in the MY00 STI is what is known as “one wire control”. This makes it difficult for an alarm (or other device) which has the customary 2 wire lock/unlock hookup.

Easy to solve...

Locate the wiring loom coming from the drivers door. Locate the white wire as shown. To test if you have correct wire do the following

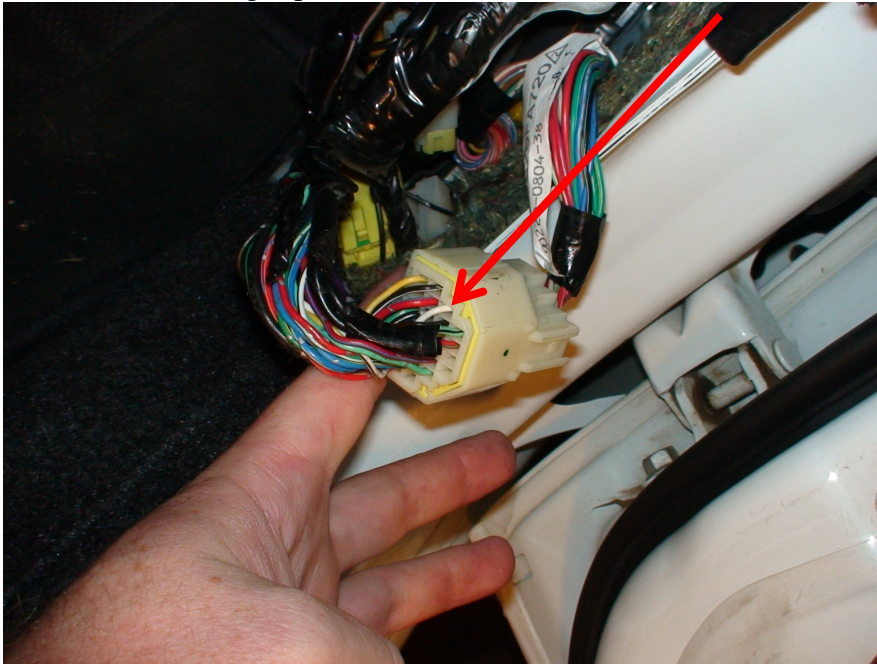1. Manually lock the doors.
2. Use a light probe or a fused wire to short it to earth. The doors should unlock



With the doors unlocked, cut the wire. The doors should lock. This proves without a doubt that you have the correct wire.

Now you can wire in a relay as per the diagram below. This will give 2 “negative” triggers. One for lock, then other for unlock. Perfect for standard alarm systems.

Note the following

- The Red line represents the white wire
- The scissors represent the cut you made.

